

Name: Aditya Meti

USN: 4NI24EC005

Date: 06-04-2026

Experiment 5

Aim: Design and analyze various op-amp circuits: i) Zero crossing detector ii) Comparator iii) inverting iv) non-inverting amplifier and v) voltage follower configurations using $\mu A741$ IC

Simulation Tool: Tina TI

Components Required: $\mu A741$ IC(Op-Amp), resistors, signal generator, battery, DMM

Schematic Circuit:

A) Zero Crossing Detector


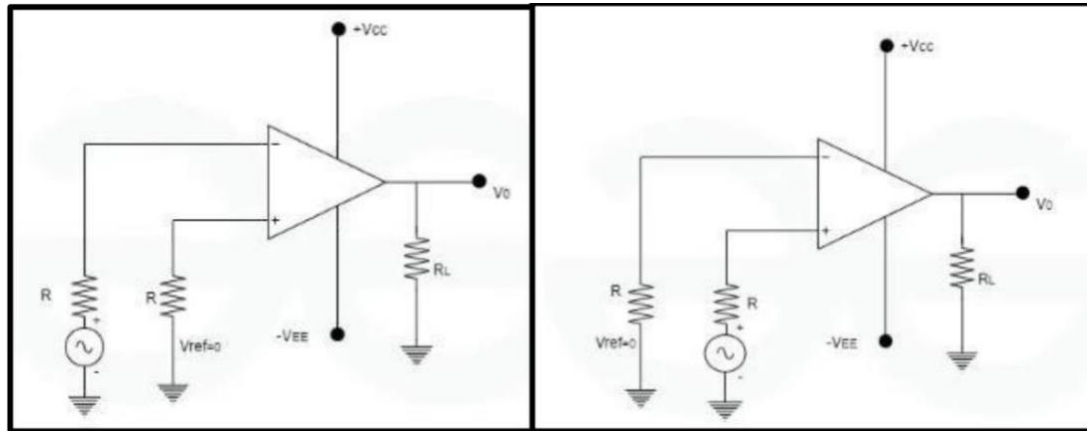


Fig. 1 a) Inverting ZCD

b) Non-inverting ZCD


1a) Inverting ZCD

Design:

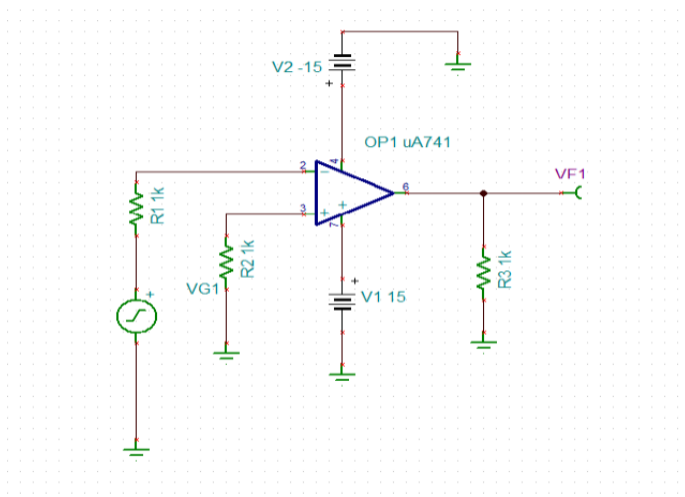


EC4L01 ANALOG CMOS IC - 2 LAB
*DEPARTMENT OF ELECTRONICS AND COMMUNICATION,
NIE, MYSORE
EVEN Semester AY 2025-26*

O/P:

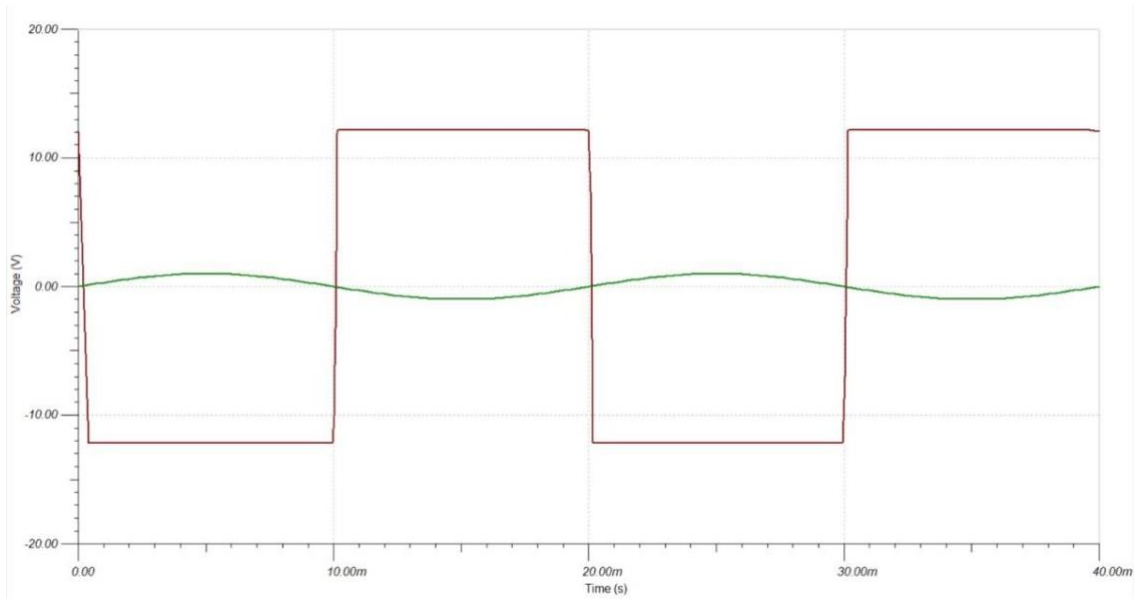


**1b) Non Inverting ZCD
Design**

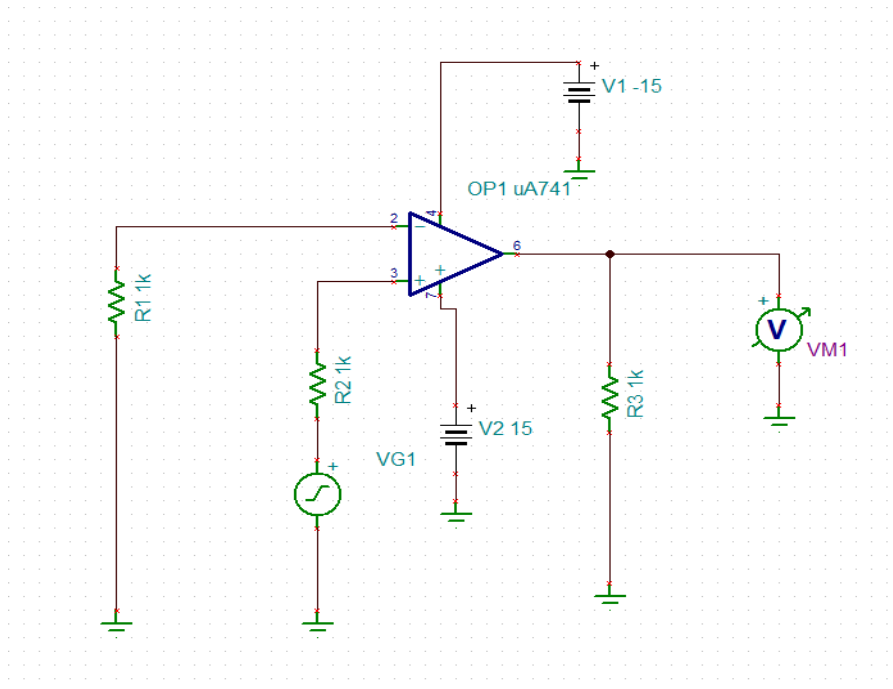


EC4L01 ANALOG CMOS IC - 2 LAB
*DEPARTMENT OF ELECTRONICS AND COMMUNICATION,
NIE, MYSORE
EVEN Semester AY 2025-26*

O/P:

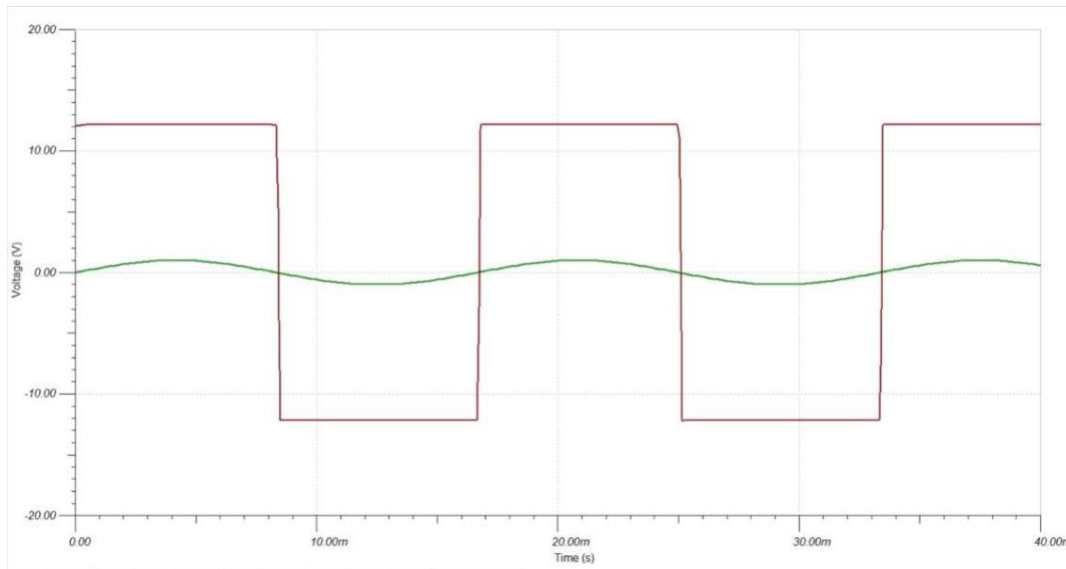

2a) Inverting Amplifier

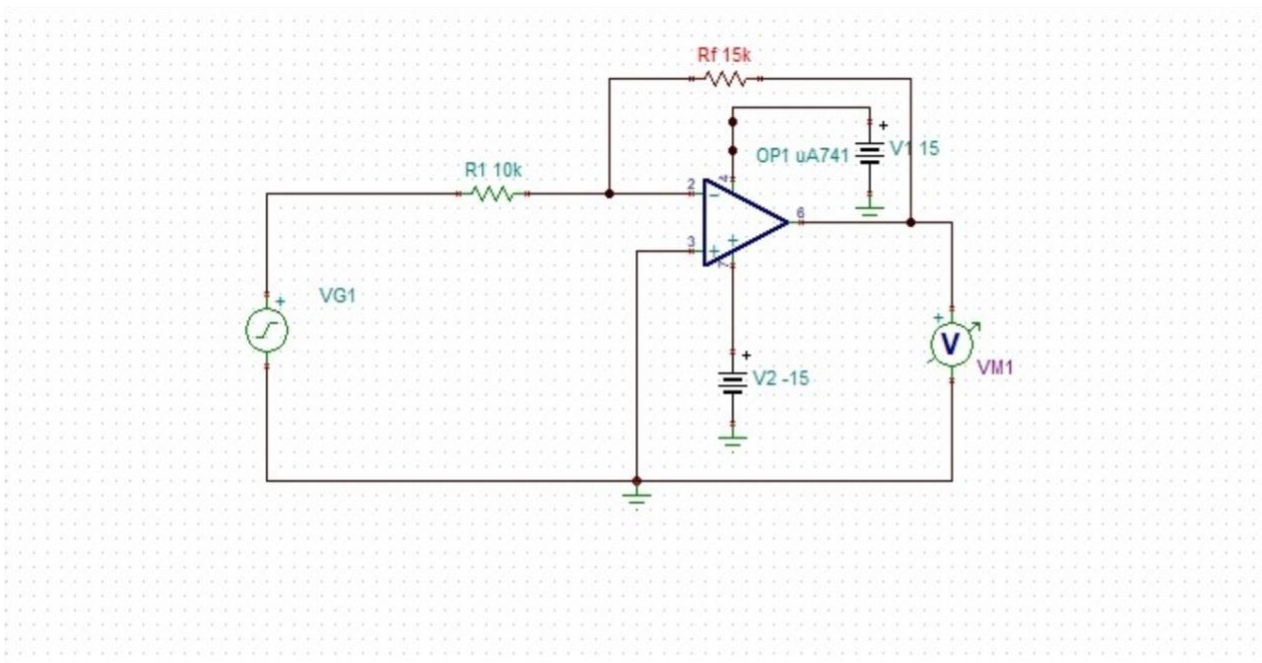
Design: $V_{out} = -1.5V_{in}$. Assume $R_f = 15k\ \Omega$ $R_i = 10k\ \Omega$



EC4L01 ANALOG CMOS IC - 2 LAB


DEPARTMENT OF ELECTRONICS AND COMMUNICATION,
NIE, MYSORE
EVEN Semester AY 2025-26

O/P:

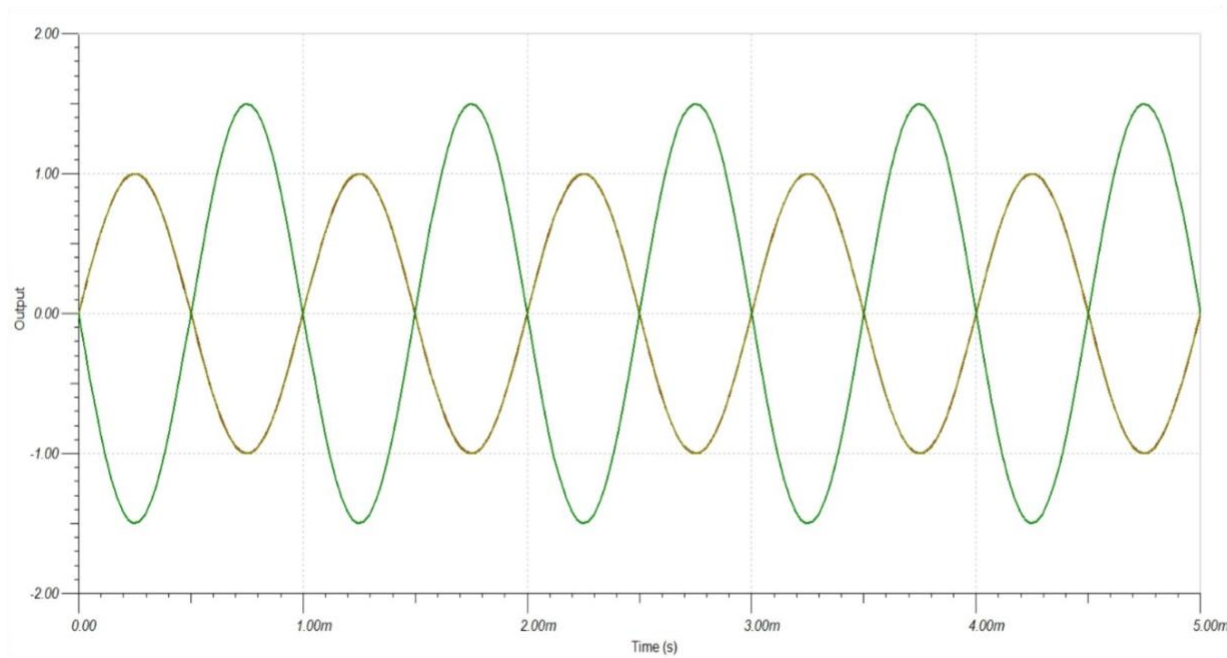

2b) Non Inverting Amplifier

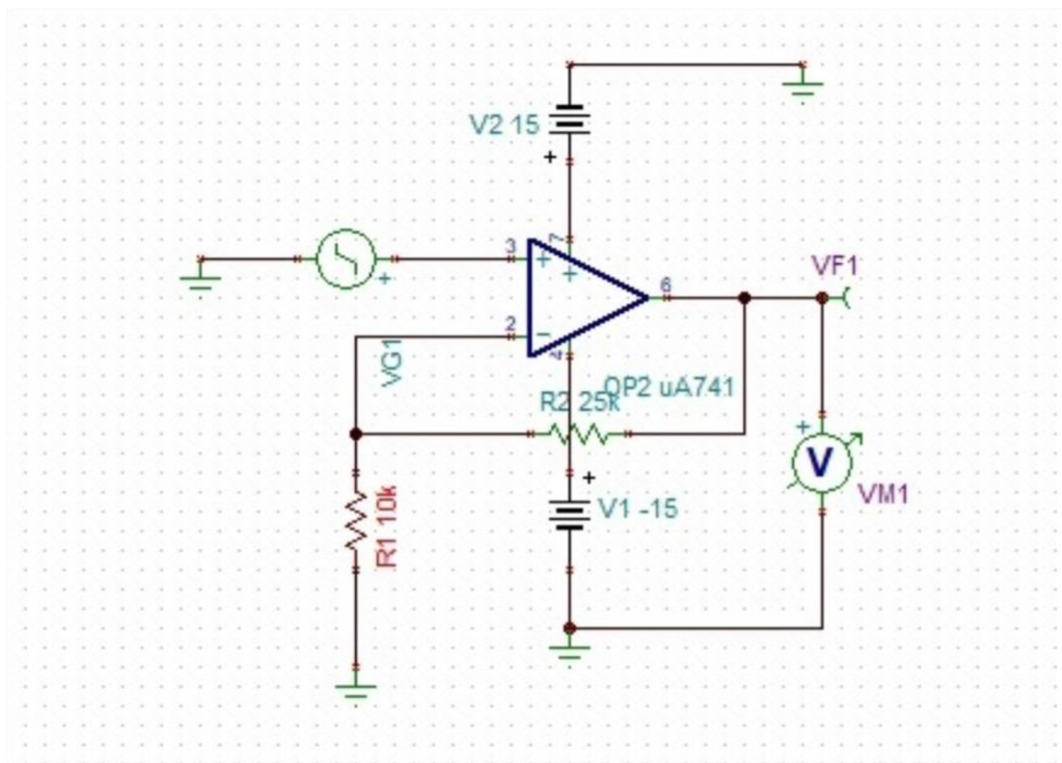
Design: $V_{out} = 3.5V_{in}$. Assume $R_f = 25k\ \Omega$ $R_1 = 10k\ \Omega$



EC4L01 ANALOG CMOS IC - 2 LAB


DEPARTMENT OF ELECTRONICS AND COMMUNICATION,
NIE, MYSORE
EVEN Semester AY 2025-26

O/P:

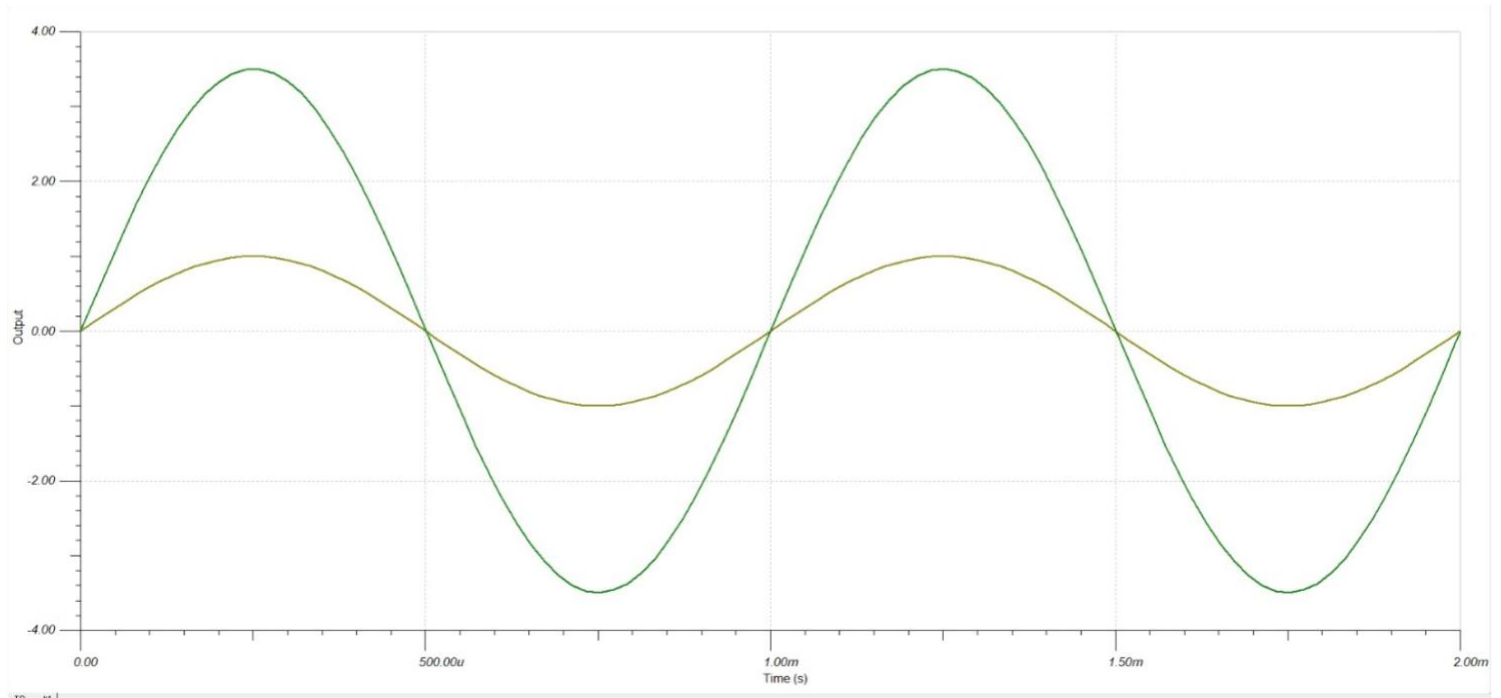

3) Voltage Follower

Design:

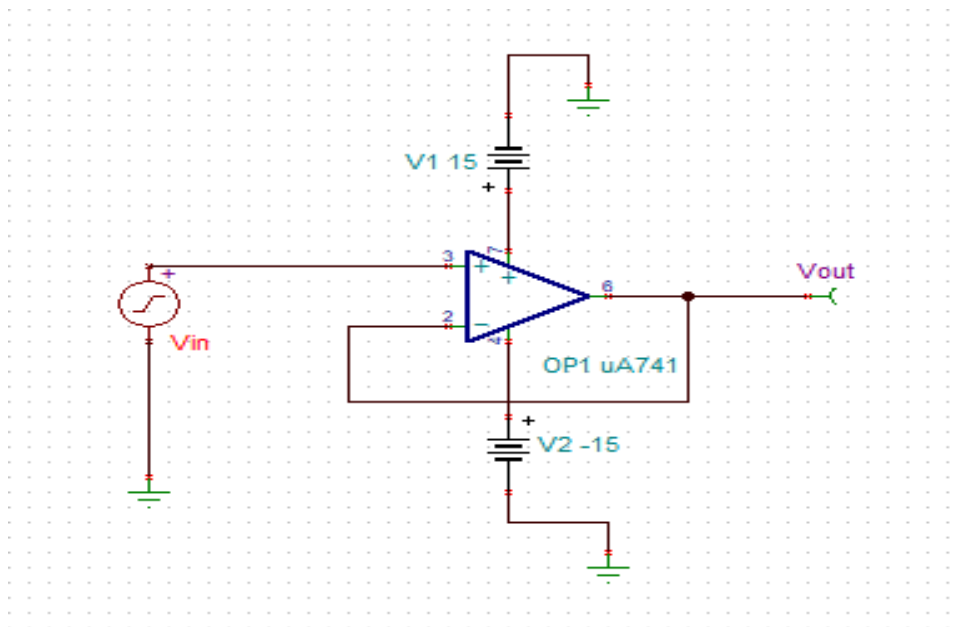


EC4L01 ANALOG CMOS IC - 2 LAB

DEPARTMENT OF ELECTRONICS AND COMMUNICATION,


NIE, MYSORE

EVEN Semester AY 2025-26

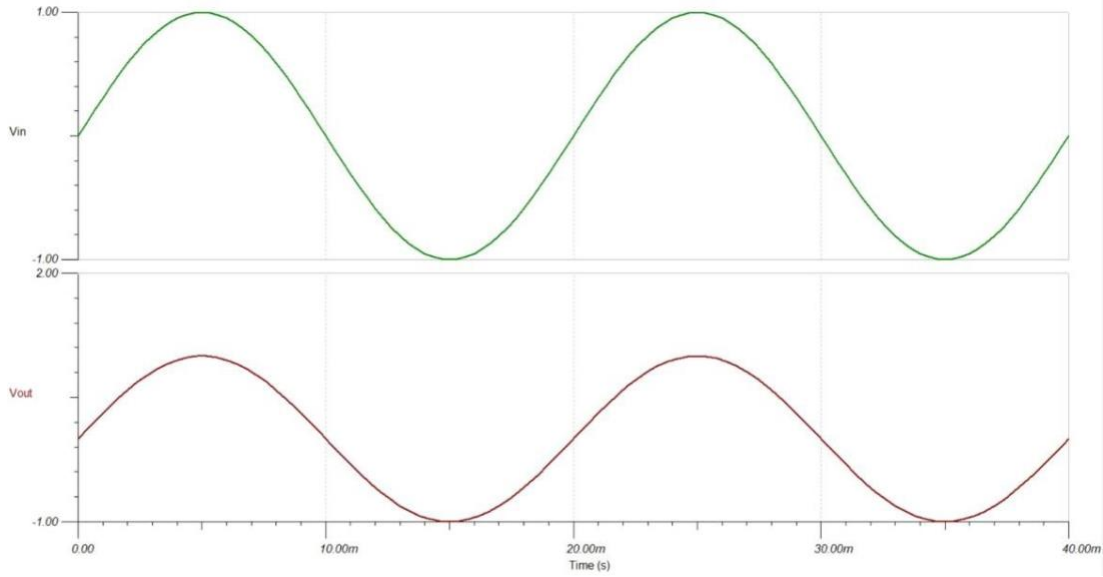


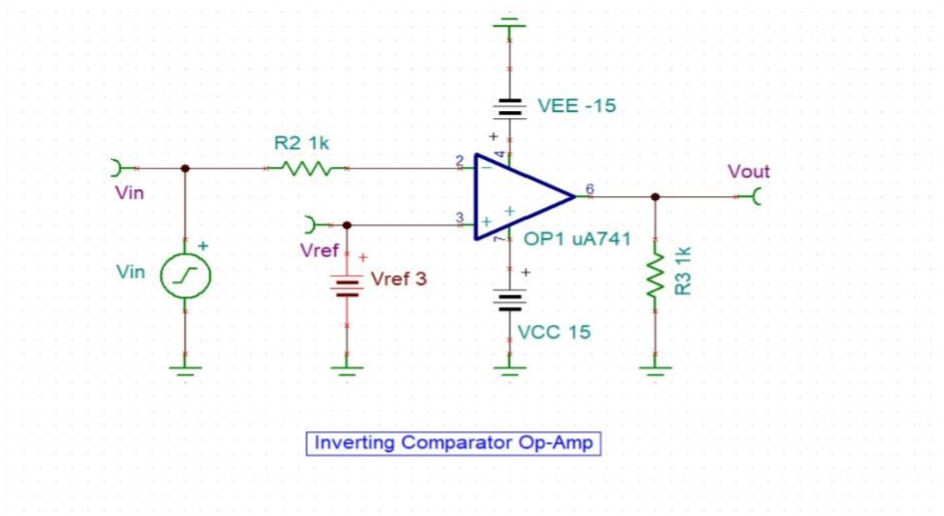4) Inverting Comparator

Design: $V_{ref}=3v$, Let's Assume $R_f=1k\ ohm$ $R_1=R_2=1k\ ohm$.



O/P:

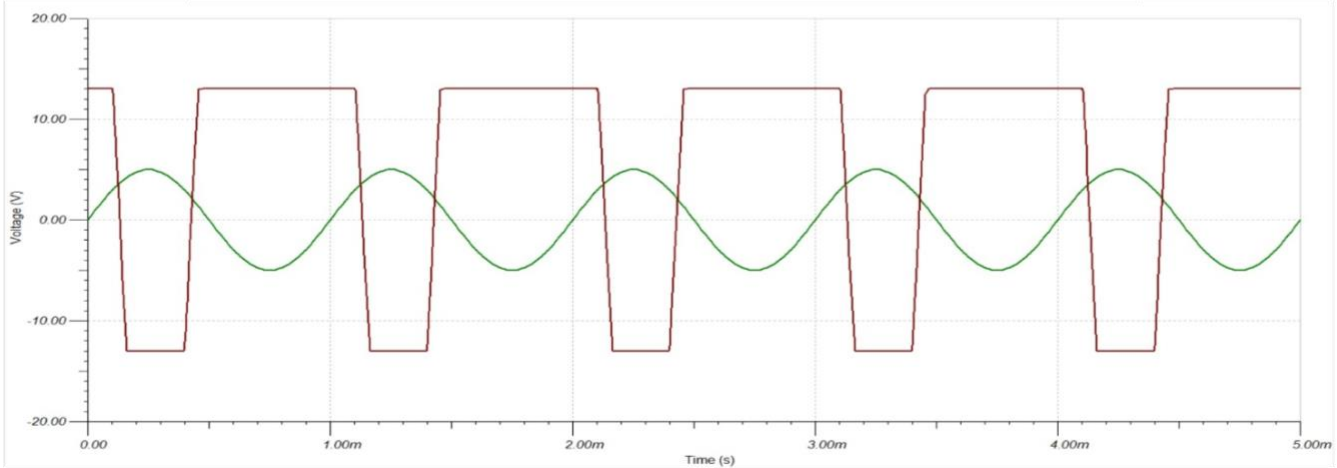


EC4L01 ANALOG CMOS IC - 2 LAB

DEPARTMENT OF ELECTRONICS AND COMMUNICATION,
NIE, MYSORE
EVEN Semester AY 2025-26

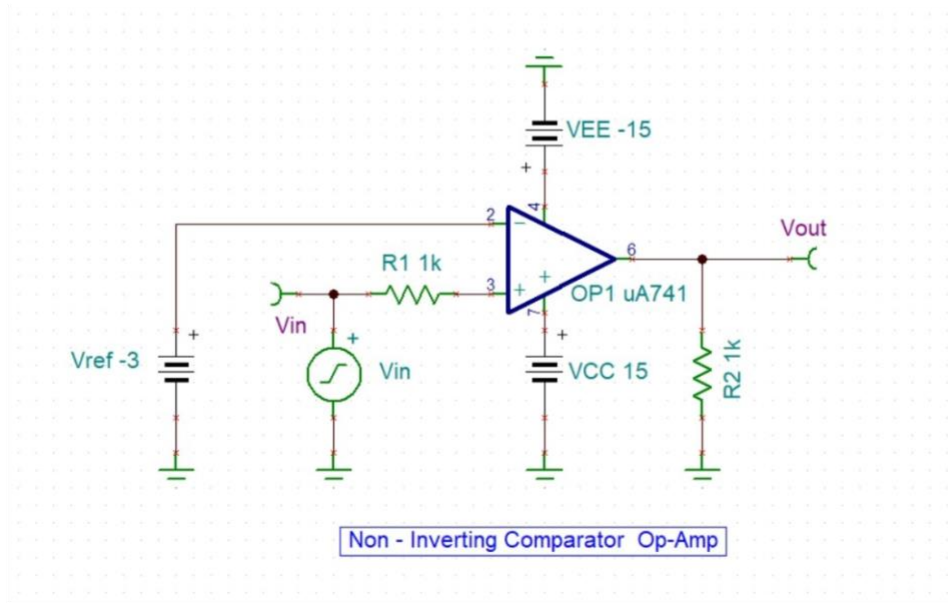
5) Non-inverting Comparator

Design:

$V_{ref} = -3V$, Let's Assume $R_f = 1k\ \Omega$ $R_1 = R_2 = 1k\ \Omega$.



O/P:

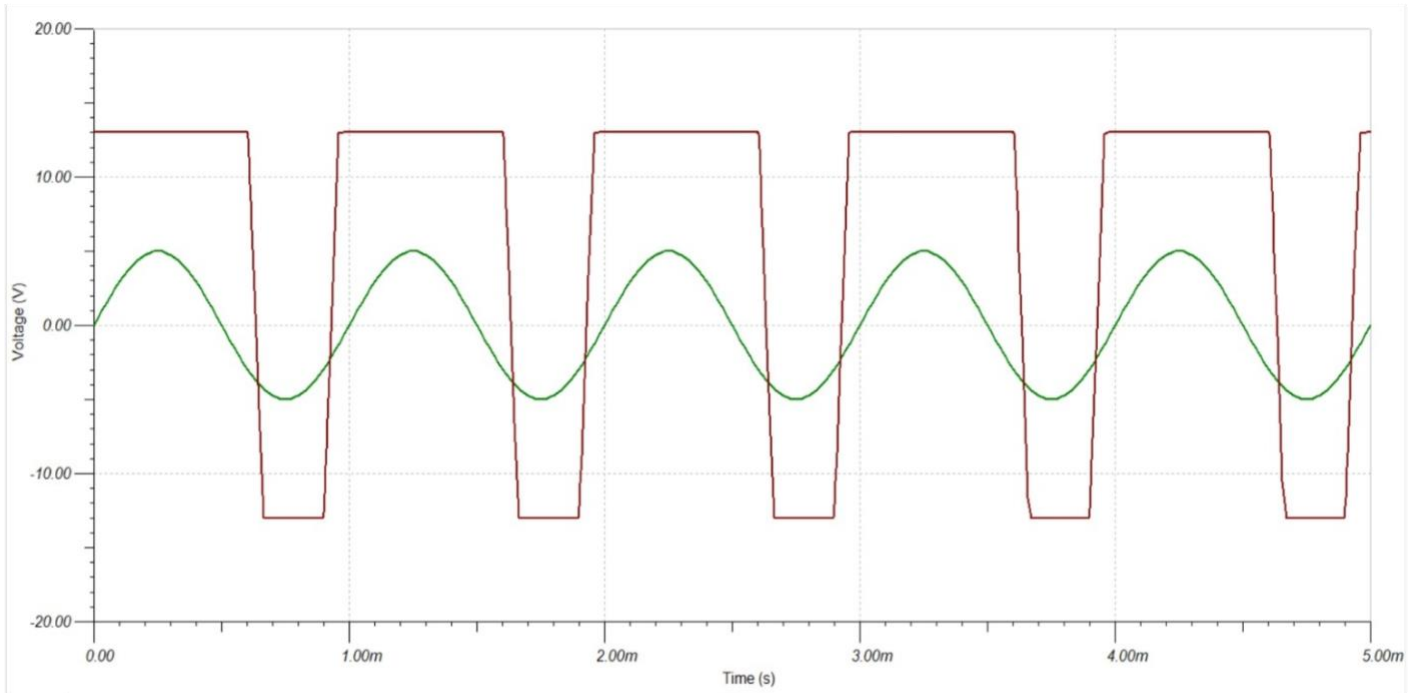

Inference:

EC4L01 ANALOG CMOS IC - 2 LAB

DEPARTMENT OF ELECTRONICS AND COMMUNICATION,

NIE, MYSORE

EVEN Semester AY 2025-26

1. The output switches exactly at the zero crossing of the input signal with sharp and nearly instantaneous transitions, confirming correct operation of the zero crossing detector, while saturating at approximately $\pm 12-13$ V instead of ± 15 V due to practical limits of the $\mu A741$ model.
2. The output is properly amplified with the expected phase relationship (180° phase shift for inverting and same phase for non-inverting), showing correct circuit operation, while the gain is close to the designed value.
3. The output closely follows the input with the same phase and nearly equal amplitude, confirming unity gain operation of the voltage follower

Result:

1. Zero crossing detector, inverting amplifier, non-inverting amplifier, and voltage follower circuits using $\mu A741$ were successfully designed and simulated in TINA-TI.
2. The obtained output waveforms verify correct switching, amplification, and buffering operations as expected.

Verified by:

Date: